1 logic gates

logic gates perform logical operations that take binary input (0s and 1s) and produce a single binary output. They are used in most electronic device including:

Table 1: logic gates

smartphones	Tablets	Memory Devices